

والتحيز

3 Selectivity  $\Rightarrow$  the ability of the receiver to reject the unwanted signals.


\* Selectivity is obtained by using Tuned Circuits and Filters

\* As the No of Filters increase the selectivity increases

\* As The Quality factor  $Q$  increase " " " "

$Q \uparrow \Rightarrow$  Selectivity  $\uparrow$

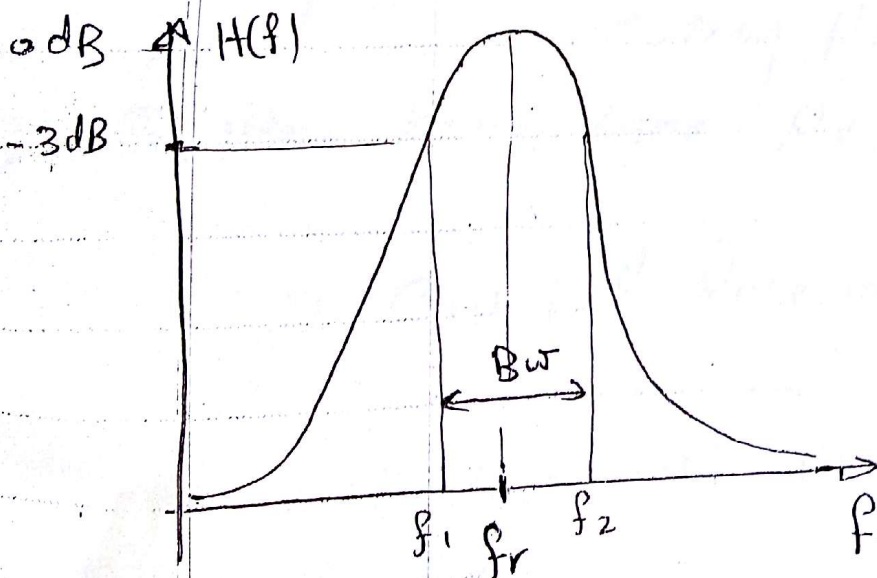\* The Bw of the tuned circuit must be wide enough to pass the signal and its sidebands, and narrow enough to eliminate the unwanted signals.



$$Bw = f_2 - f_1$$

$$Bw = \frac{f_r}{Q}$$

## 2] Sensitivity

the ability of the Rx to <sup>feel</sup>sense and amplify the weak signals.

\* The higher the amplifier gain the high the Rx selectivity

\* High gain receiver is obtained by using multiple amplification stages

### Types of Receivers

- ① Crystal Receiver
- ② tuned Radio Frequency Rx,
- ③ Super heterodyne Rx,

### Crystal Receiver

هوا بطن أنواع ال Rx AM و بطن

#### ① tuned circuit

which provide the selectivity such


that the Rx can separate the desired signals from the unwanted signals



② envelope detector;

Consist of Diode (Crystal) and Capacitor  
Serve as AM De Modulator

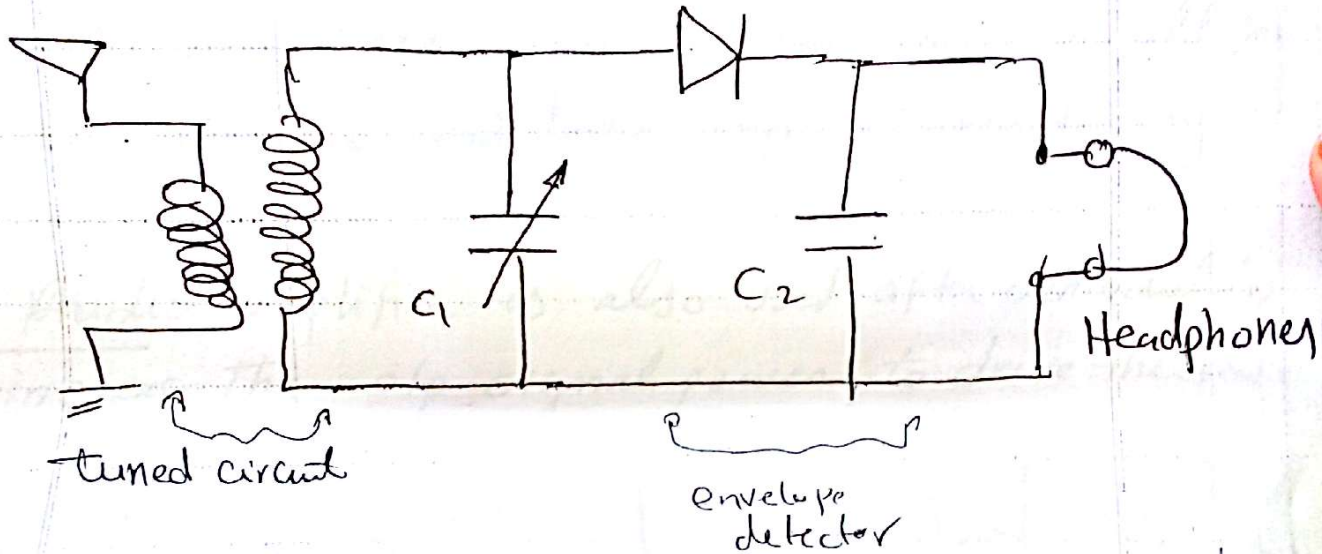③ earphone, to reproduce the received audio signal.



## ② Tuned Radio Frequency (TRF) Receiver

وهو نظام إمدت النظام 1 لاسلكي في النظام 2 لاسلكي  
يعاني من بعض العيوب وهي


- ① low sensitivity  $\Rightarrow$  No Amplifier
  - ② poor selectivity  $\Rightarrow$  only one tuned circuit
- ولذلك السلكي تر عمل (TRF) Rx حيث تر من سلكي  
التردد لاسلكي

## TRF Rx

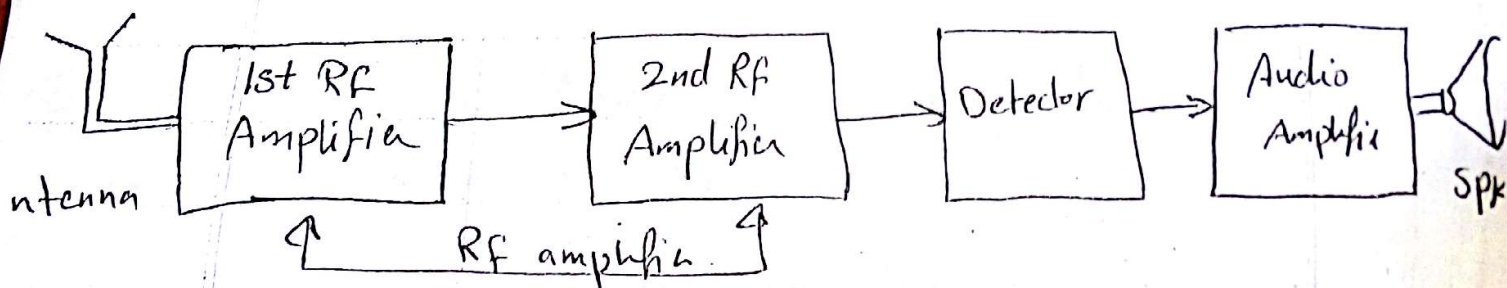a) Sensitivity improvement by using groups of RF amplifiers between the antenna and the detector.

\* The RF amplifiers stage increase the over all gain of the receiver and hence, improve sensitivity

\* An Audio amplifier is also used after demodulator to increase the o/p signal power to drive the speaker




b) Selectivity improvement

⇒ By using multiple tuned circuit with RF amplifiers.

\* the greater the tuned circuit the narrower the Bandwidth

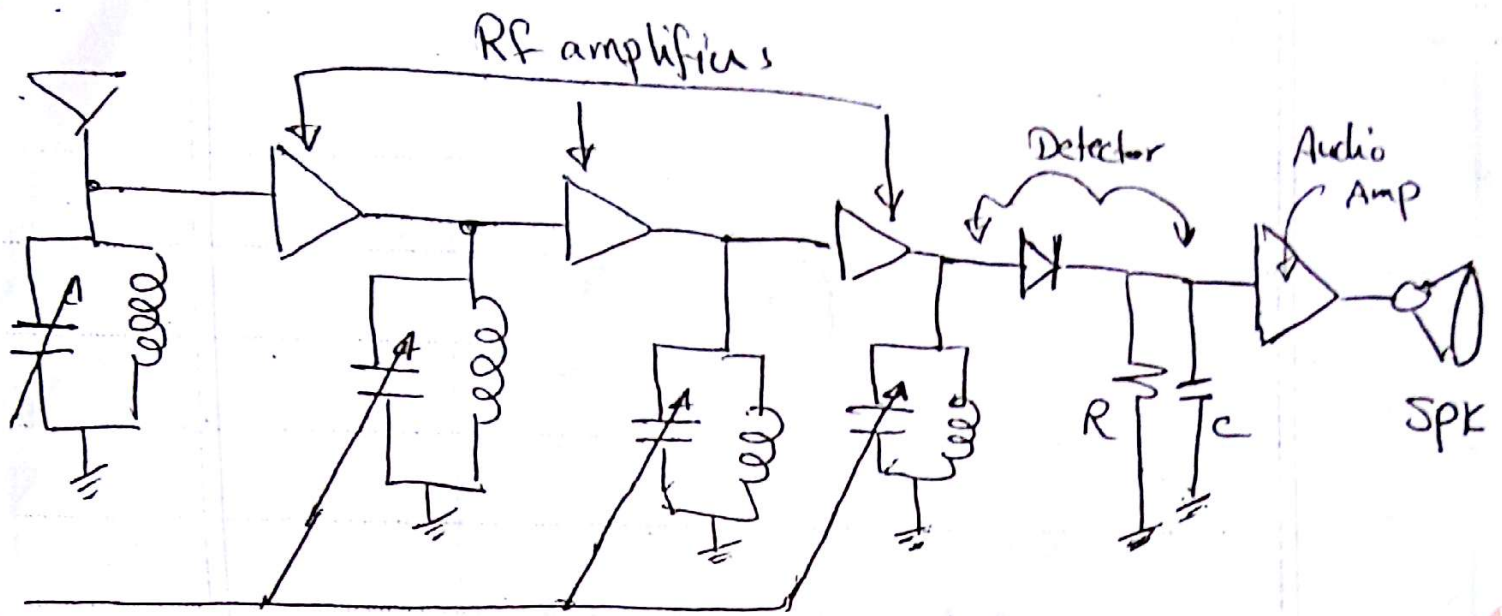\* All the tuned circuit are variable to select the desired signal as shown in the figure





## Disadvantage of TRF Receiver

- ① the selectivity of the tuned circuits is vary with the frequency.
- ② using multiple tuned circuit may be affect the desired received signal.




## ③ Super-heterodyne Receiver

هذا النظام من قلب على جميع المسائل

\* hetro  $\Rightarrow$  translation to another frequency.  
 dynamic  $\Rightarrow$  amplification of the detected signal  
 Super  $\Rightarrow$  from (super sonic) which means the heterodyn  
 is above the audio freq. 7 range.
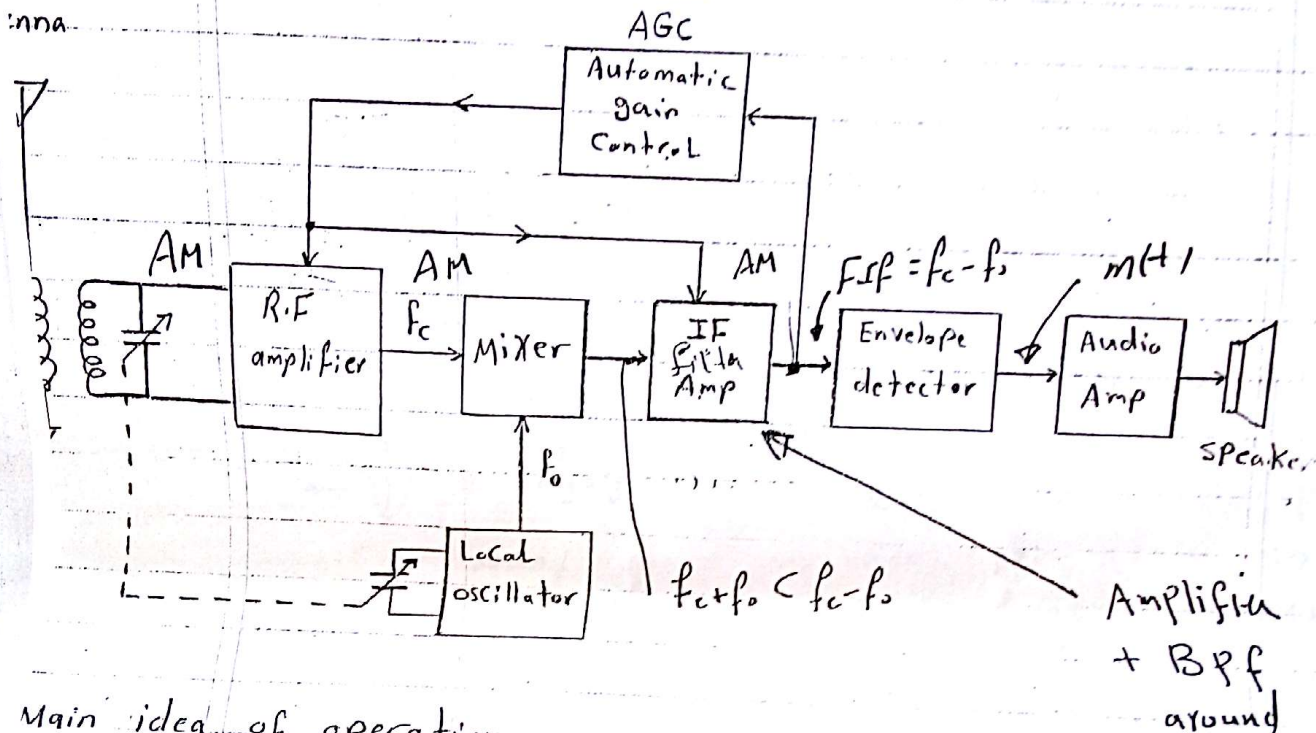
### 3) Superhetrodyne Receiver Block diagram



Main idea of operation :-

- The superhetrodyne receiver takes the incoming radio frequency signals whose frequencies varies from station to another and transform them into a fixed frequency called intermediate frequency (IF).  $= f_{if}$

So that we get fixed receiver performance for all different signals.

يقوم بتحويل ترددات الإشارات المتغيرة (  $f_{c1}, f_{c2}, \dots, f_{cn}$  ) إلى تردد واحد فقط ثابت يسمى (  $f_{if}$  ) ثم يقوم بعمل demodulation وذلك نظراً لقلة الخسارة للتردد لكل المحطات أو الإشارات المتغيرة

Mixer

$$f_{c_i} \rightarrow \otimes \rightarrow f_{if} = f_c - f_o = 455 \text{ KHz for AM}$$

مختلج  
التردد المحلي



## operation


- 1] The antenna converts the received EM waves into electrical RF signals.
- 2] The tuned (LC) RF amplifier is properly tuned by varying the capacitor value to select the desired signal frequency ( $f_c$ ).

• it also provides sufficient amplification for the radio signal by RF Amplifier

- 3] The local oscillator frequency ( $f_o$ ) is tuned by varying the oscillator capacitor

the oscillator capacitor is coupled with the RF amplifier capacitor, and tuned together at the same time.

- 4] mixing →

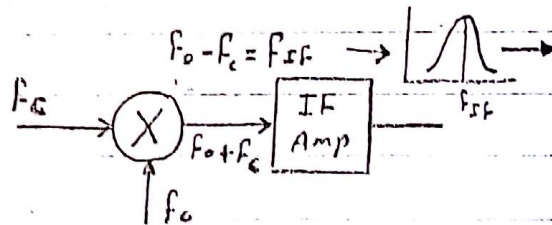

The received signal frequency ( $f_c$ ) is mixed with the tuned local oscillator frequency ( $f_o$ ) to give a fixed frequency difference known as intermediate frequency  $f_{if}$

$$f_o - f_c = f_{if}$$

عکس

For AM

$$f_{if} = 455 \text{ KHz}$$

(9)


The mixer op will contain sum and difference freq,

$$f_o + f_c \text{ } f_o - f_c$$

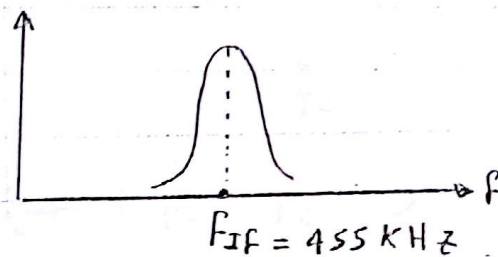(9)

[5] The IF amplifier is tuned to pass only the difference frequency ( $f_o - f_c$ ) that equals the  $f_{IF} = 455 \text{ kHz}$ .

and reject all other frequencies ( $f_o + f_c$  &  ~~$f_o - f_c$~~ )



• The IF amplifier amplifies the signal and provides more selectivity.  $\rightarrow$  ~~input~~ ~~output~~ ~~response~~

[6] The output of the IF amplifier is fed to the envelope detector to recover the original signal. «mtt»

[7] The recovered signal is then amplified by the audio amplifier to a level sufficient to drive the loudspeaker.

[8] AGC  $\rightarrow$


\* the near stations will have high power level while the far or distant stations will have lower power level.

To get fixed power level for all stations we use AGC circuit to adjust the gains of RF and IF amplifiers to provide a signal with fixed power level to the envelope detector.


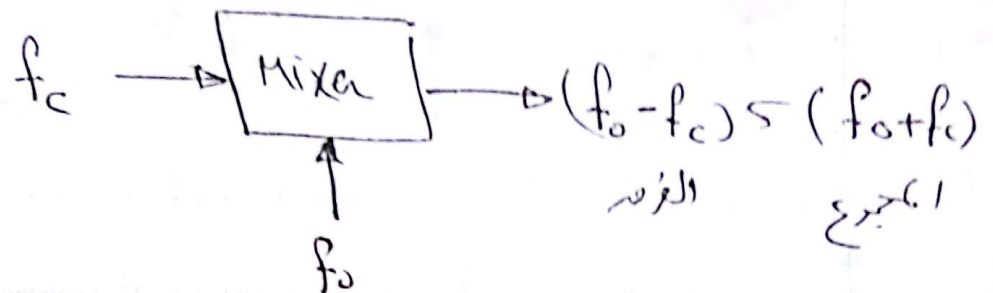
## Mixer operation


يقوم الـ Mixer بجمع تردد  $f_0$  و تردد  $f_c$  لإنتاج



\* لكي يخرج عبارة عن التردد  $f_0 \leftarrow f_c$  حيث  $f_0 > f_c$  وذلك عن طريق الجمع  $f_0 + f_c$

## IF Amplifier

يقوم الـ BPF بتمرير التردد فقط



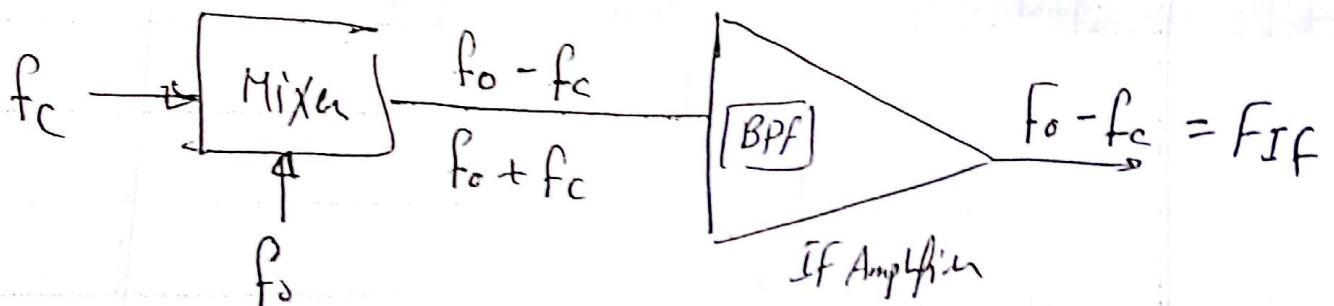


$$\therefore \boxed{\text{IF Amp O/P} = f_0 - f_c = FIF}$$

$FIF = 455 \text{ KHz}$  for AM

هذا ذكر خلاف ذلك

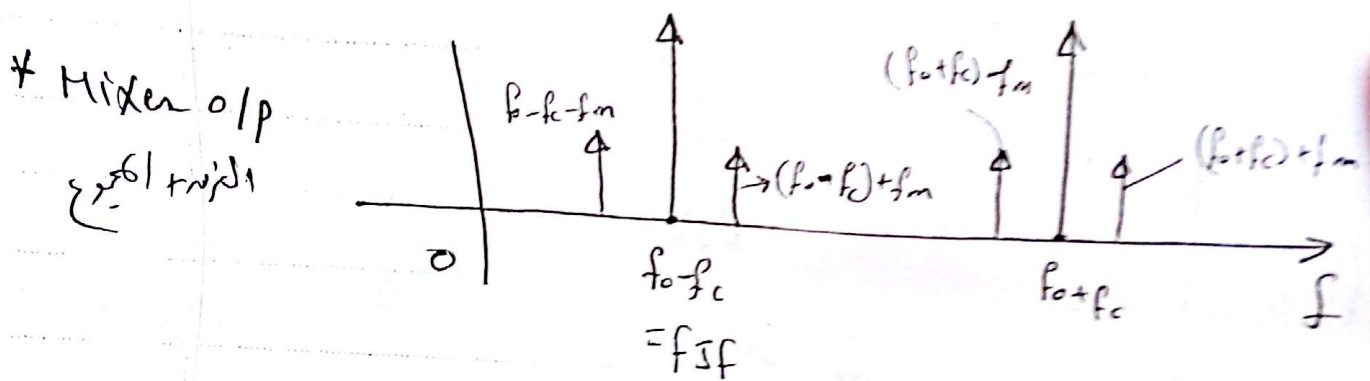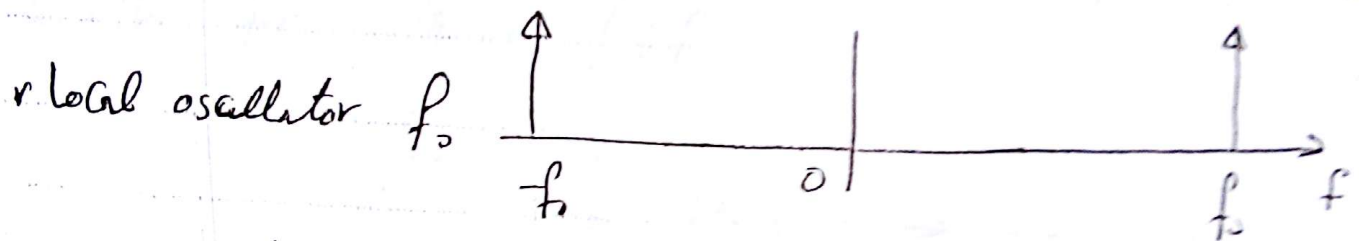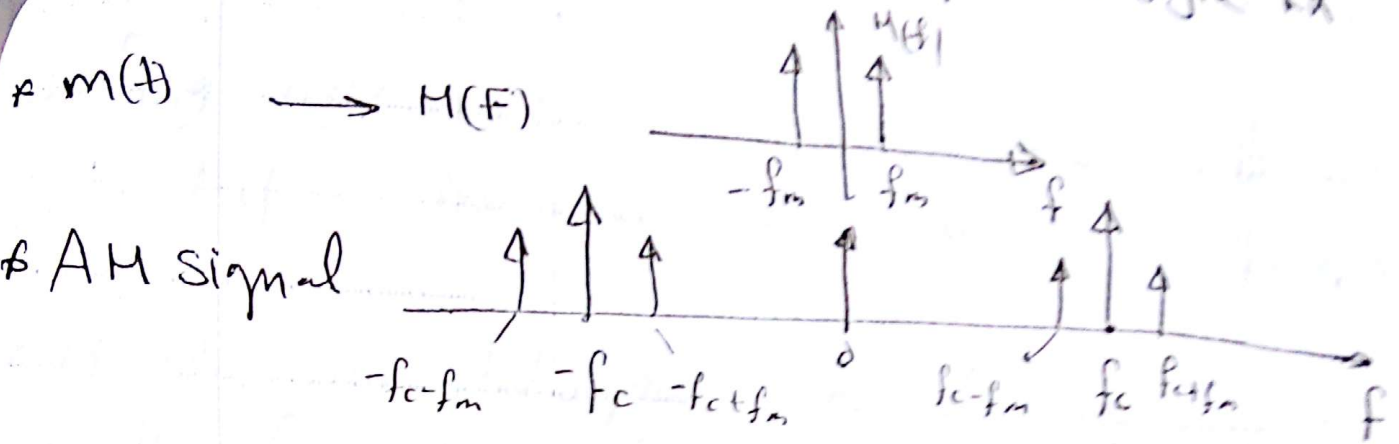
spectrum of all signals at Super heterodyne Rx



\* IF Amplifier


o/p

المزيج المعزز

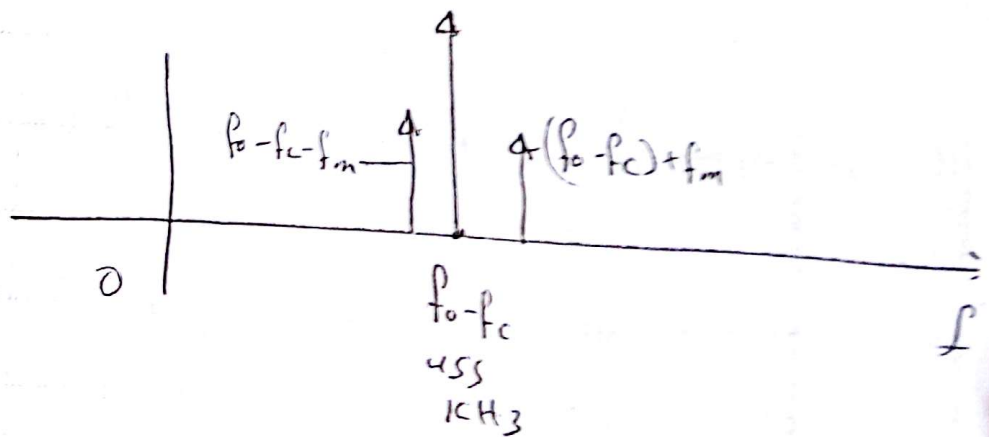

\* Detector o/p

$m(t)$

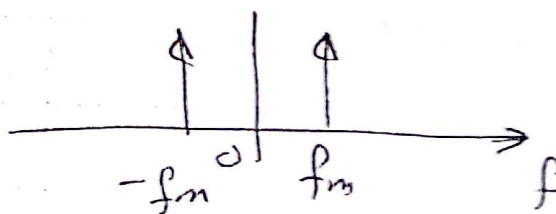



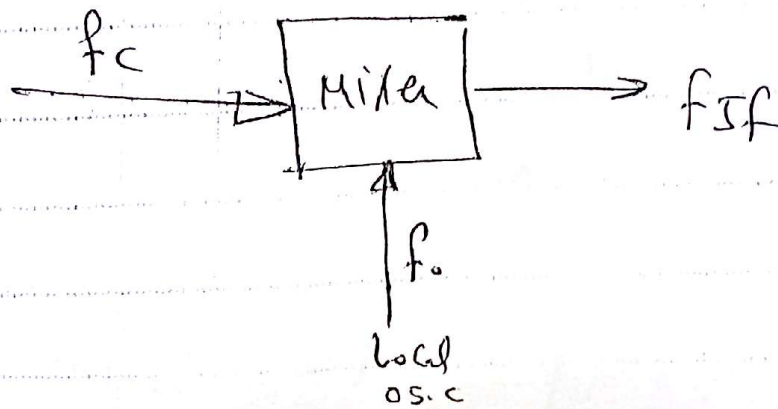
# Image frequency

هناك أي إشارة غير مرغوب فيها تردد  $f_{\text{imag}}$  في Mix مع Local oscillator  $f_{\text{LO}}$  give  $f_{\text{IF}}$

is any unwanted signal when its frequency mix with  $f_{\text{LO}}$  give  $f_{\text{IF}}$



$$f_{\text{IF}} = f_o - f_c$$

$$f_o > f_c \Rightarrow$$

$$f_o = f_c + f_{\text{IF}}$$

$$f_{\text{IF}} = f_c \text{ or } f_o$$

$$f_{\text{imag}} = f_c + 2f_{\text{IF}}$$

$$\text{or } f_{\text{imag}} = f_o + f_{\text{IF}}$$

و

والتي في كل مرة

التي هي في كل مرة

poor tuned circuit

|| من اشارة (Antenna)

UP Side Conversion

$$f_o > f_c$$

$$f_{IF} = f_o - f_c$$

$$f_{imag} = f_c + 2f_{IF}$$

$$= f_o + f_{IF}$$

Down side Conversion

$$f_c > f_o$$

$$f_{IF} = f_c - f_o \rightarrow \text{الخروج}$$


$$f_{imag} = f_c - 2f_{IF}$$

$$= f_o - f_{IF}$$

نarrow band tuned circuit  $f_c$  image  
 حيث  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   $f_c$   
 BW  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   
 Image  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$


$$BW = \Delta F_{RF} < 2f_{IF}$$

tuned circuit

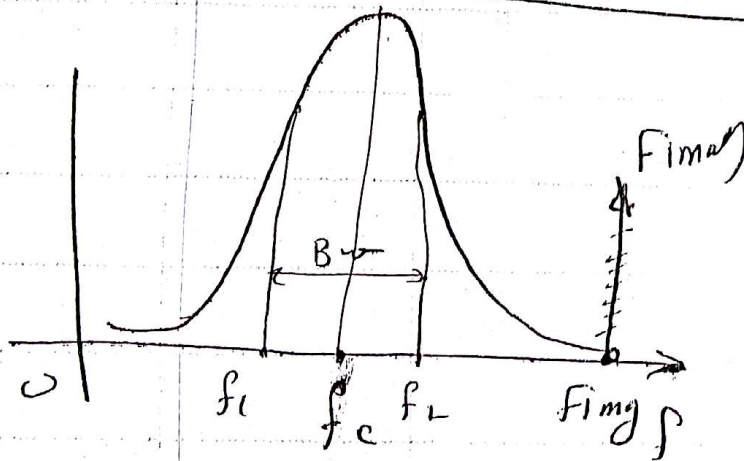

$$BW = f_2 - f_1 = \Delta F_{RF} < 2f_{IF}$$

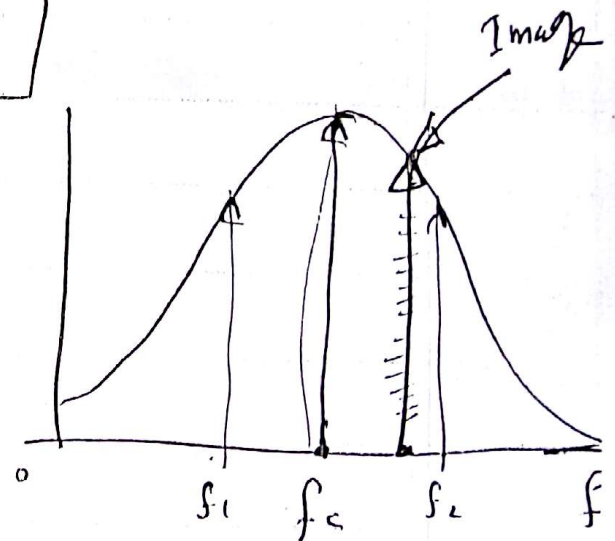حيث  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   
 BW  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   
 Image  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$




$$BW > 2f_{IF}$$

حيث  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   
 BW  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$   
 Image  $f_c$   $f_o$   $f_{IF}$   $f_{imag}$



## ③ Superhetrodyne Receiver

(191)

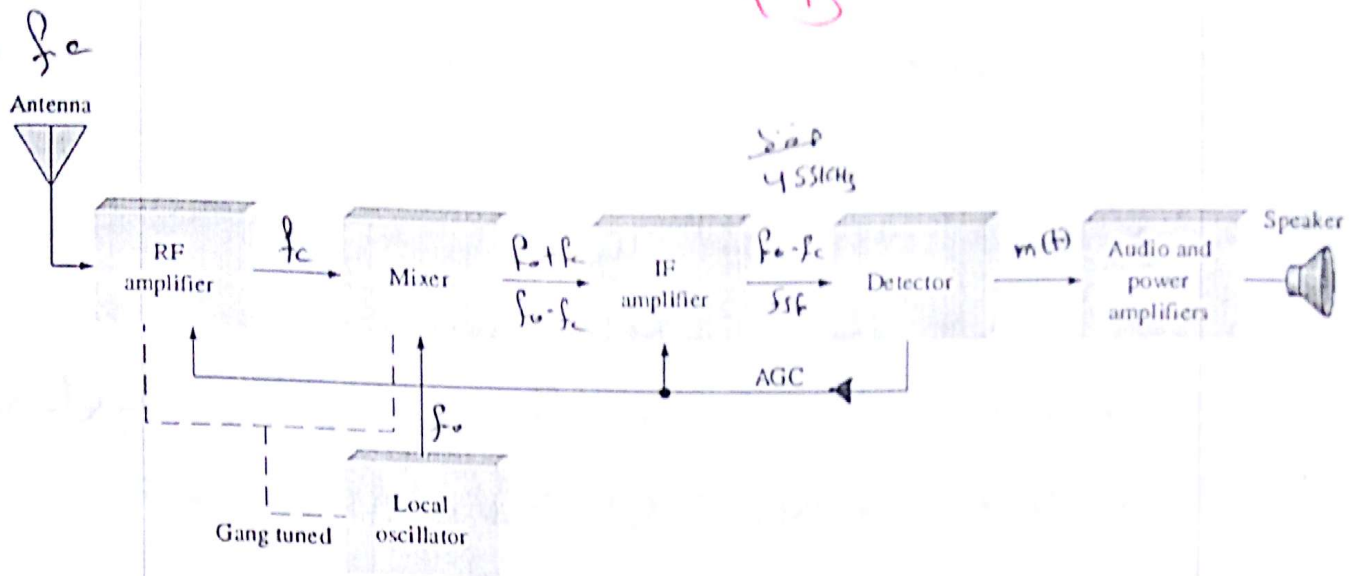

### Main idea of operation

\* the Superhetrodyne RX takes the incoming radio frequency signal ~~and~~ ( $f_c$ ) and transform it to fixed frequency called intermediate frequency  $f_{if}$

$$\left. \begin{array}{l} f_{if} = 455 \text{ KHz} \rightarrow \text{AM} \\ f_{if} = 10.7 \text{ MHz} \rightarrow \text{FM} \end{array} \right\} \text{fixed}$$

\* So we get fixed performance for all received signals

یعنی ہمیں یکساں کارکردگی کے لیے تمام ریسیو کی گئی فیکوئنسیوں ( $f_c$ ) کو ایک ہی فیکوئنسی  $f_{if}$  پر تبدیل کر دیتے ہیں اور اس سے بہتر کارکردگی ملتی ہے

$$f_c \rightarrow \text{Mixer} \xrightarrow{f_o} f_o - f_c = f_{if}$$

(8)

Super heterodyne Receiver

$\otimes$  Antenna  $\Rightarrow \approx \sqrt{Z_0} \left( \frac{V}{I} \right) = \sqrt{\frac{60}{\lambda}} R_{rad}$

① Rf Amplifier:

high freq Amplifier  $\Rightarrow$  حساسیت بالا  
sensitivity  $\Rightarrow$  حساسیت بالا

Variable Rf tuned Circuit سے متعلقہ  
اختیار رکھنے کی صلاحیت و عمل reject  
selectivity

② Mixer  $\Rightarrow$  mix الكاد  $f_c < f_o$  و  $f_o$  هو  
المرسول في الغرض و  $f_o - f_c$  و  $f_o + f_c$  الجميع

• الصوت الرئيس من ال Mixer هو الغمز  
هو تردد ثابت والمقام من قيسه وتقسيم ال  
 $f_{IF} = f_o - f_c$  والنز  
Rx performance

③ Local oscillator


Variable oscillator مع  $f_c$  Mix مع  $f_c$

$\times$  يتم التحكم في كلاً من  $f_0$  و  $f_c$  الذي تم اختياره مع  
طريقة الـ RF tuned circuit ~~من نفس الوقت~~ بحيث يكون دائماً

9
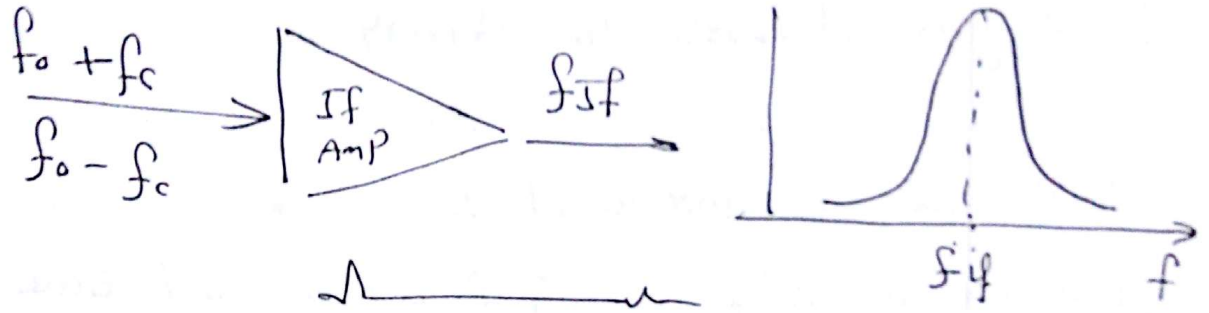
## If Amplifier

- هو عبارة عن Amplifier تكبر الإشارة وكذلك يكون على If filter لكي يمر الفهر فقط ويزيد فيه selectivity



## ⑤ Detector →

هو عبارة عن envelope detector، مصمم لاستخراج الإشارة  $m(t)$  من آخر

## ⑥ Audio Amplifier →

هو مصمم لرفع مستوى الصوت البارد في الإشارة  $m(t)$  من تشغيل السماع

## ⑦ Automatic Gain Control AGC


يقوم بتحكم في Gain كلاً من If and Rf Amplifiers بحيث تضمن أن مستوى الإشارة الذي يصل إلى Detector ثابت وبالتالي يكون مستوى الإشارة للمحطات البعيدة هو نفسه لمحطات الأقرب


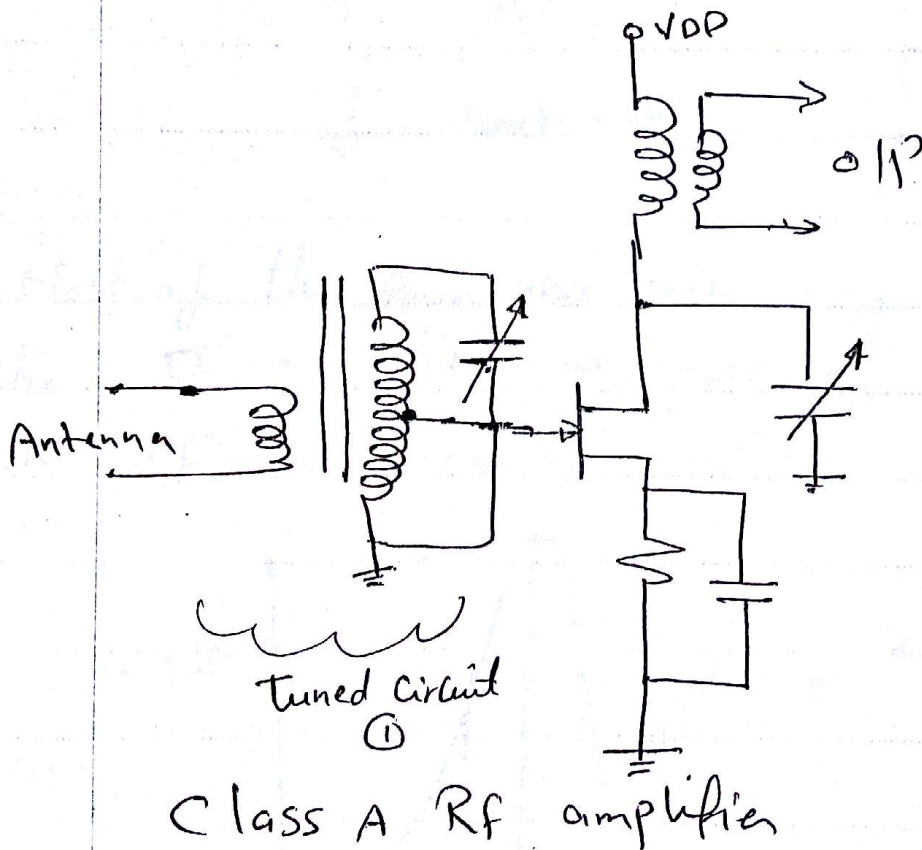
# Superhetrodyne AM Rx

lect 2

- ① RF amplifier  $\Rightarrow$  Provide high gain to improve Sensitivity.  
 $\Rightarrow$  Provide high selectivity using tuned Circuit  
 $\Rightarrow$  Called Low noise amplifier (LNA)  
 $\Rightarrow$  Consist of class A power amplifier  $\Rightarrow$  for linearity.  
 $\Rightarrow$  Circuits contain BJT or FET Transistor




تuned circuit  
 Class A RF amplifier


①
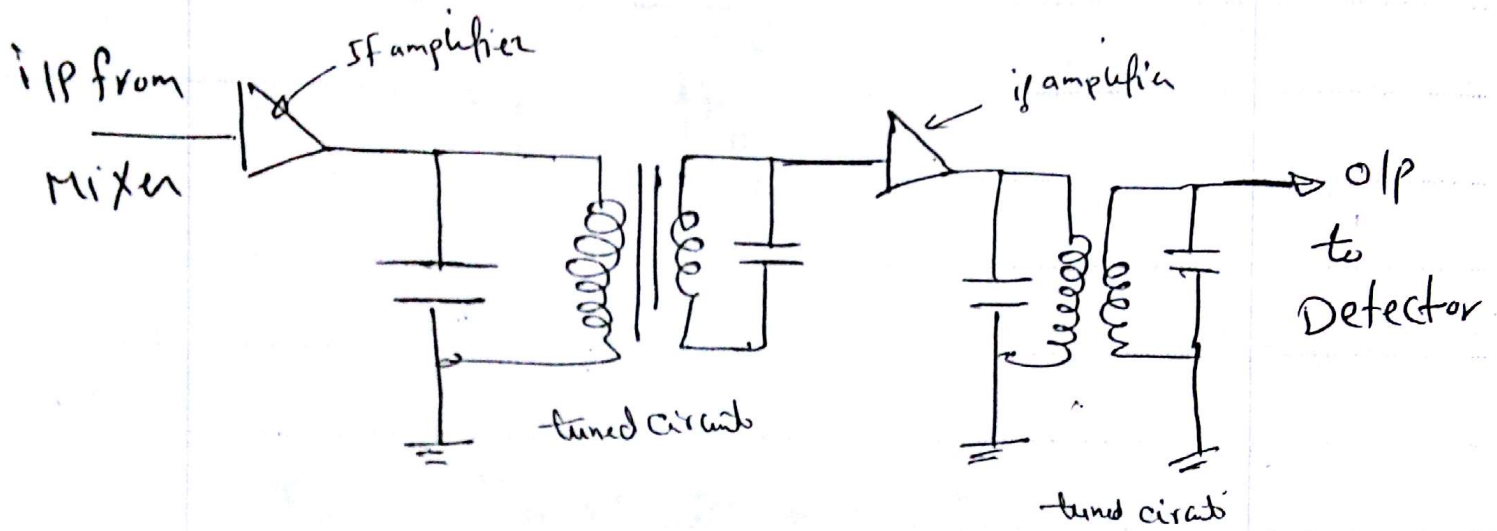
## IF Amplifier :

- \* Respond only to 455kHz and any side frequencies lying in the 10kHz Bandwidth
- ⇒ has a tuned circuit at its i/p or o/p centered at 455kHz with 10kHz BW



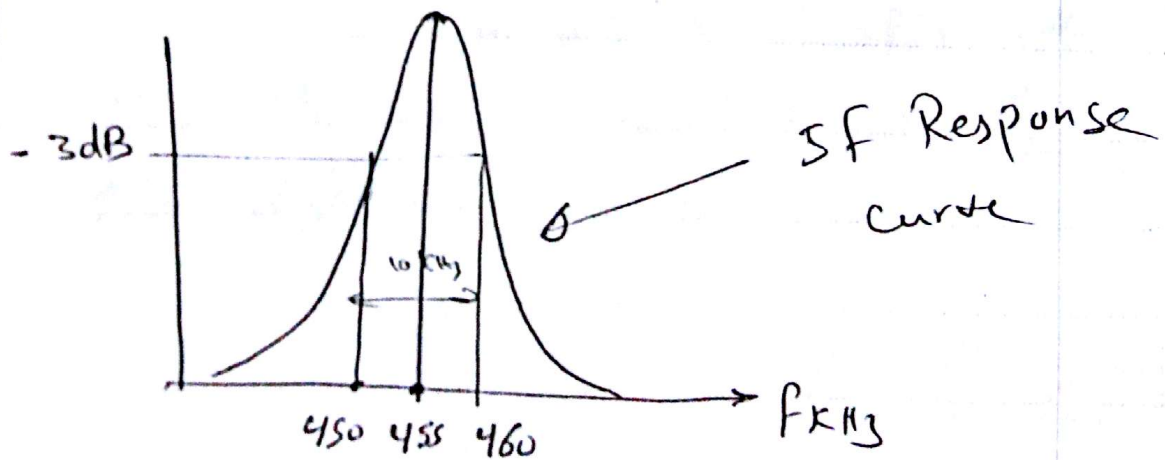- \* Most of the gain and selectivity are produced by the IF amplifier
- So we use two or more IF amplifiers



BW = 10kHz for AM


2



Mixer,

Nonlinearity  
Diode Mixer

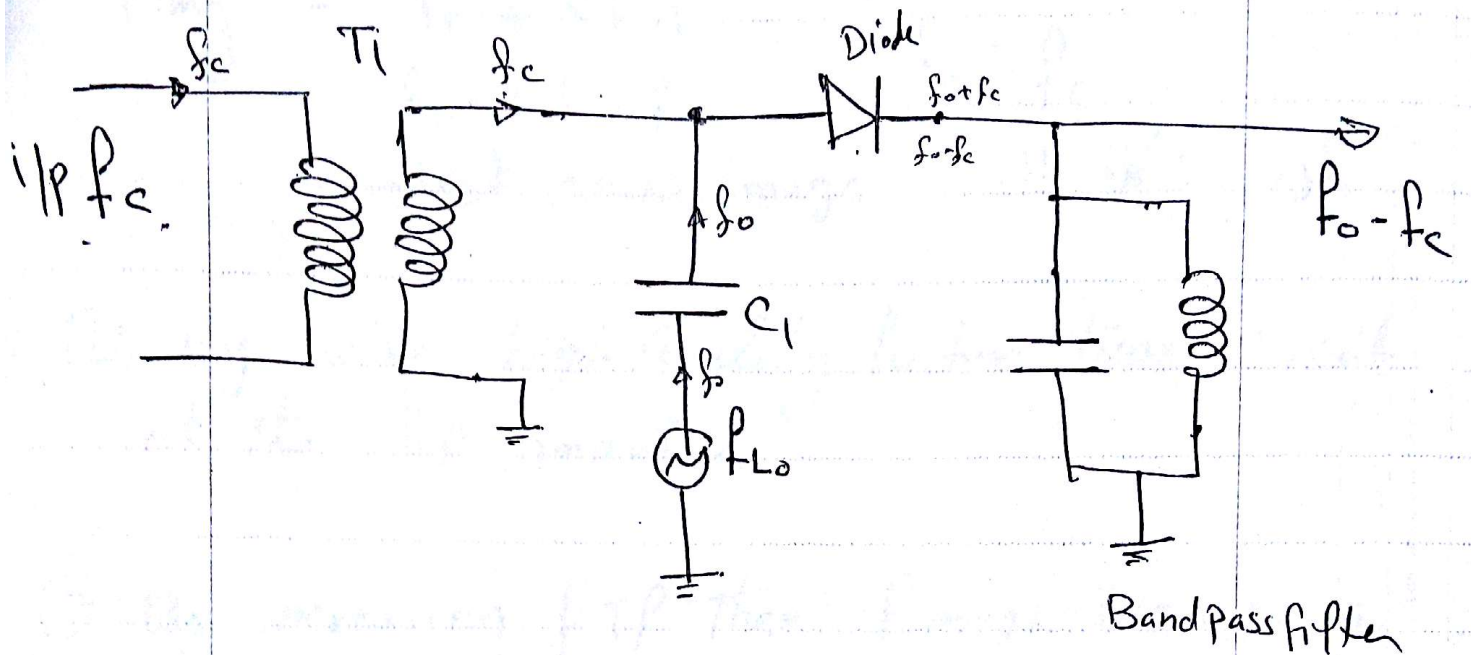التيار غير خطي في دايود  
التيار غير الخطي هو



التيار غير الخطي في دايود  $f_c$  والتيار غير الخطي في دايود  $T_1$


التيار غير الخطي في دايود  $f_o$  والتيار غير الخطي في دايود  $C_1$

التيار غير الخطي في دايود  $f_c$  والتيار غير الخطي في دايود  $f_o$

التيار غير الخطي في دايود  $f_c$  والتيار غير الخطي في دايود  $f_o$  والتيار غير الخطي في دايود  $f_c$

$(f_o - f_c) < (f_o + f_c)$

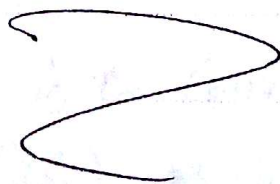then the tuned circuit select only  
the difference  $f_o - f_c$



## Solving image Problem

$$f_{\text{img}} = f_c + 2f_{\text{IF}} \quad \leftarrow f_o > f_c$$

$f_o + f_{\text{IF}}$       image       $f_o - f_{\text{IF}}$

~~~~~ طيف ~~~~~ طيف ~~~~~

① By using high quality factor tuned circuit at the RF amplifier

② By increasing  $f_{\text{IF}}$  then  $f_{\text{image}}$  increase & tuned circuit

~~~~~ طيف ~~~~~ طيف ~~~~~

+ وضاع كل شيء وهو أفضل من الكل البقية عن طريق

### Dual-Conversion Receiver


Local oscillator (LO) و Mixer (M)

⇒ The first Mixer Convert the incoming signal ( $f_c$ ) to a high intermediate frequency  $F_{\text{IF}_1}$  to eliminate image

⇒ The second Mixer is to Convert the first ( $F_{\text{IF}_1}$ ) to lower frequency ( $F_{\text{IF}_2}$ ) as shown in the figure

Demodulator



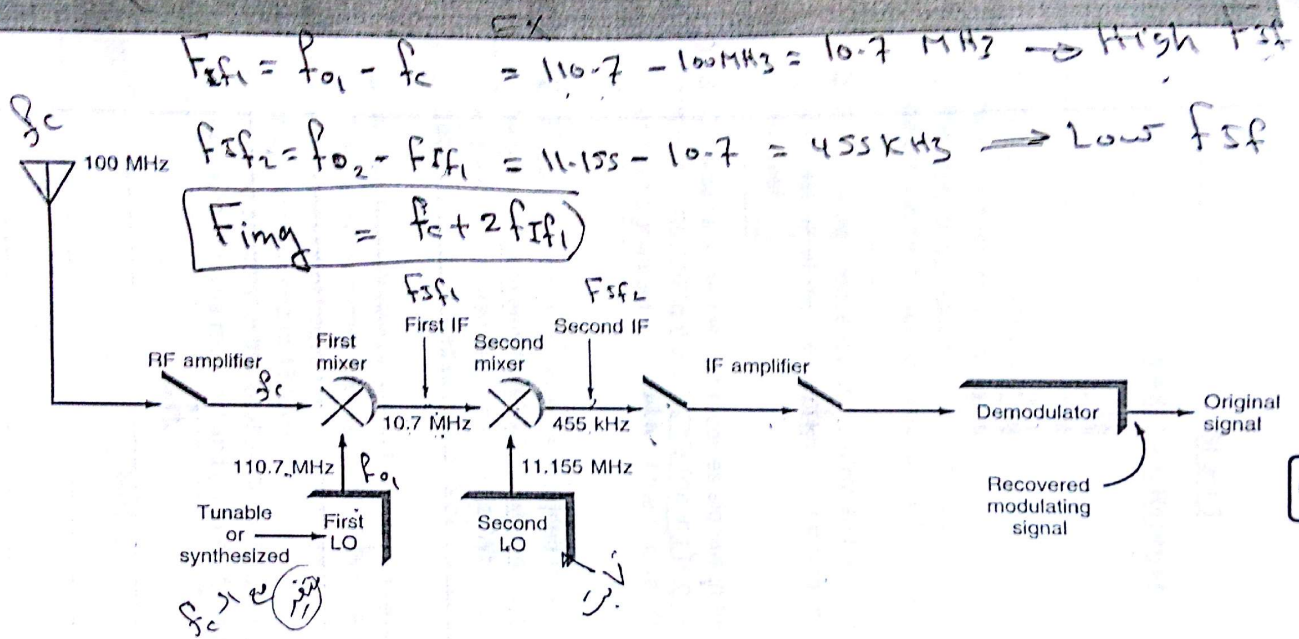

### A dual-conversion superheterodyne

- ①  $f_{o1}$  سے پہلے RF tuned circuit اور  $f_c$  اس سے پہلے  
 ②  $f_{o2}$  ثابت ہے  $f_{sf2} < f_{sf1}$  کو ثابت  
 ③  $F_{img} = f_c + 2F_{sf1}$  "  $f_c$  اور  $f_{sf1}$  کے درمیان  
 اور  $f_{img} = f_c + 2F_{sf1}$

### Sheet 3

#### BASIC Am Receiver


1. The input to a certain AM receiver consists of a 1500 kHz carrier and two side frequencies separated from the carrier by 20 kHz. Determine the frequency spectrum at the output of the mixer amplifier and determine the frequency spectrum at the output of the IF amplifier.
2. For a carrier frequency of 1.2 MHz and a modulating frequency of 8.5 kHz, list all of the frequencies on the output of the mixer in an AM receiver.
3. Consider a superhet that receives signals in the 50-54MHz range with  $f_{lo}=f_c+f_{if}$ . Assuming there is little filtering prior to the mixer, what range of input signals will be received if the  $f_{if}$  is (a) 455 kHz. (b) 7MHz.
4. A superheterodyne receiver is designed to receive signals with carrier frequencies between 4 and 6 MHz with transmitted bandwidths of 100 kHz each. Its IF frequency is 850 kHz. What range of local oscillator frequencies is required using high-side injection ( $f_{LO} > f_c$ ) ?
5. A radio receiver used in the AM system is shown below. The mixer translates the carrier frequency  $f_c$  to a fixed IF of 455 kHz by using a local oscillator of frequency  $f_{LO}$ . The broadcast-band frequencies range from 540kHz to 1600kHz. Determine the range of tuning that must be provided in the local oscillator (i) when  $f_{LO}$  is higher than  $f_c$  (superheterodyne receiver) and (ii) when  $f_{LO}$  is lower than  $f_c$ .



# Sheet 3 - AM Rx

Q)  $f_c = 1500 \text{ KHz}$      $f_m = 20 \text{ KHz}$

SOL

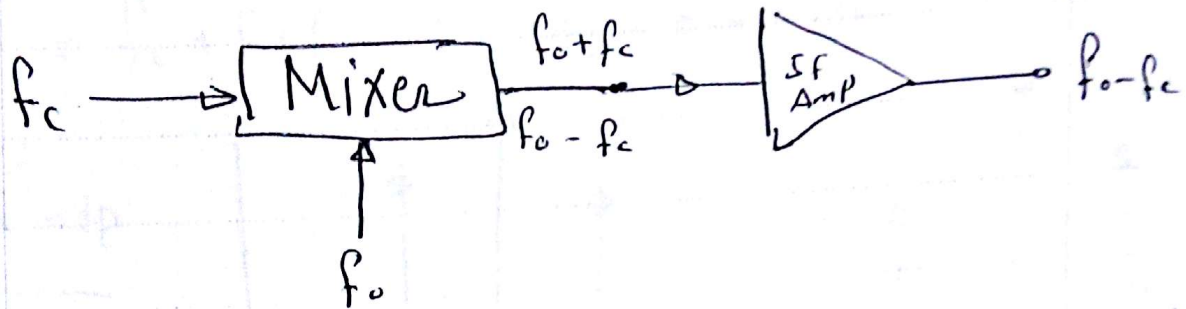


Let  $f_{if} = 455 \text{ KHz}$

$f_o = f_c + f_{if} = 1500 + 455 = 1955 \text{ KHz}$


At Mixer o/p

الترددات الخارجة

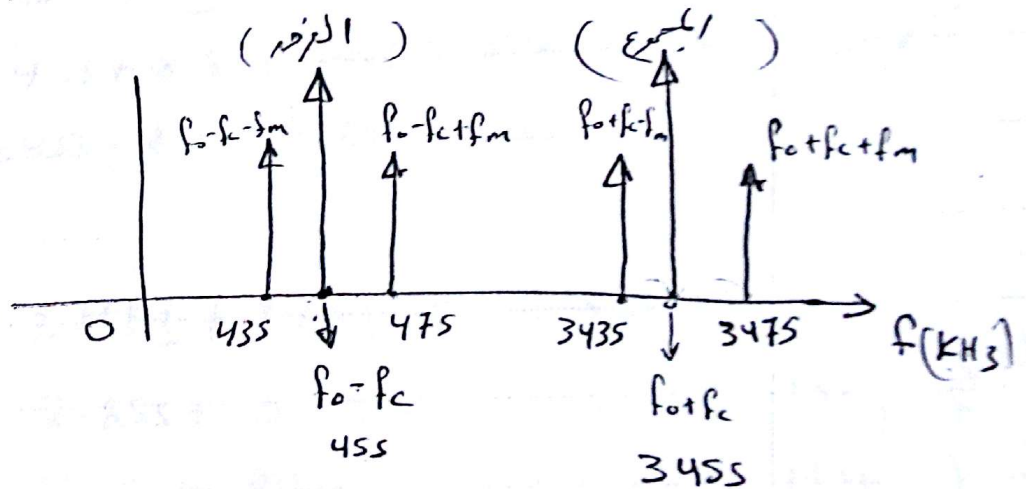

At IF Amp o/p

الترددات الخارجة

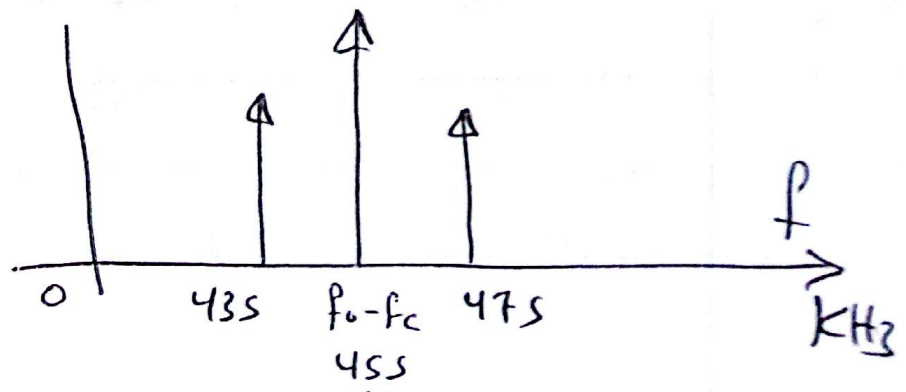


$$f_c = 1.2 \text{ MHz} \quad f_m = 8.5 \text{ kHz}$$

SOL

$$\text{Let } f_{IF} = 455 \text{ kHz}$$

$$f_o = f_c + f_{IF} = 1.2 \text{ MHz} + 0.455 \text{ MHz} = 1.655 \text{ MHz}$$

Mixer o/p

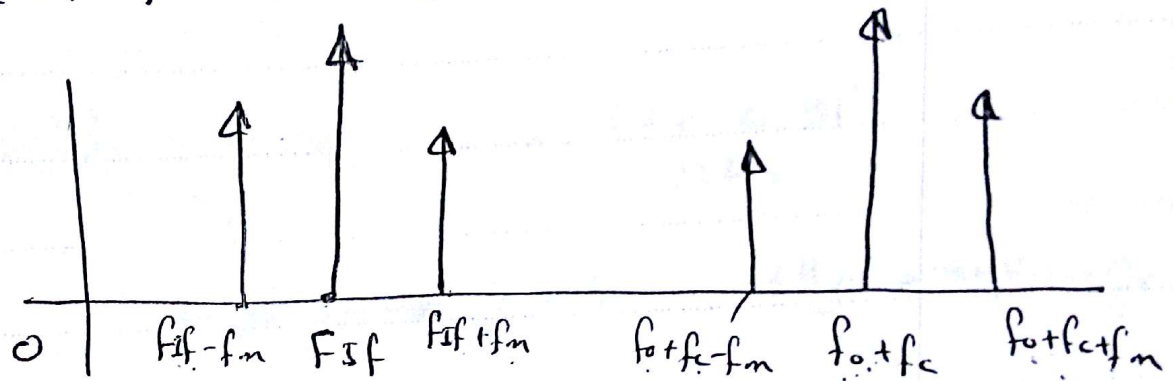

$$1) f_{IF} = 455 \text{ kHz} = f_o - f_c$$

$$2) f_{IF} + f_m = 455 + 8.5 = 463.5 \text{ kHz}$$

$$3) f_{IF} - f_m = 455 - 8.5 = 446.5 \text{ kHz}$$

الفرق

$$4) f_o + f_c = 1.2 \text{ MHz} + 1.655 = 2.855 \text{ MHz}$$

$$5) f_o + f_c + f_m = 2.855 + 8.5 \text{ kHz} = 2.8635 \text{ MHz}$$

$$6) f_o + f_c - f_m = 2.855 - 8.5 \text{ kHz} = 2.8465 \text{ MHz}$$

$$f_c = (50 - 54 \text{ MHz}) \leftarrow \text{little filter} \Rightarrow \text{image}$$

SOL

a)  $f_{if} = 455 \text{ kHz}$

circ  
bad tuned  
circuit

$$f_{\text{imag}} = f_c + 2f_{if} = (50 \rightarrow 54) + 2 \times 455 \text{ kHz}$$

$$= (50 + 0.91) \text{ MHz} \rightarrow (54 + 0.91) \text{ MHz}$$

$$= 50.91 \rightarrow 54.91 \text{ MHz} \rightarrow \text{image range}$$

$\therefore$  New Range of Received signal  $(50 \rightarrow 54.91) \text{ MHz}$



b) for  $f_{if} = 7 \text{ MHz}$

$$f_{\text{imag}} = f_c + 2f_{if} = (50 \rightarrow 54) + 2 \times 7$$

$$= 50 + 14 \rightarrow 54 + 14$$

$$= 64 \rightarrow 68 \text{ MHz} \rightarrow \text{image range}$$

$\therefore$  The Range of ip signal  $(50 \rightarrow 68) \text{ MHz}$



$$f_c = (4 \rightarrow 6) \text{ MHz} < f_m = 100 \text{ kHz} \quad \text{r} \quad f_{IF} = 850 \text{ kHz}$$

SOL

for high side injection ( $f_{LO} > f_c$ )

$$f_o = f_c + f_{IF}$$

$$= (4 \rightarrow 6) + 850 \text{ kHz}$$

$$f_o = 4.85 \rightarrow 6.85 \text{ MHz}$$



$$\textcircled{5} \quad f_{IF} = 455 \text{ kHz} \quad f_{LO} = ??$$

$$f_c = (540 \rightarrow 1600) \text{ kHz}$$

SOL

a) for  $f_{LO} > f_c$

$$f_{LO} = f_o = f_c + f_{IF} = (540 \rightarrow 1600) + 455$$

$$f_o = (540 + 455 \rightarrow 1600 + 455)$$

$$f_o = (995 \rightarrow 2055) \text{ kHz}$$



b) for  $f_o < f_c$

$$f_o = f_c - f_{IF} = (540 - 455) \rightarrow (1600 - 455)$$

$$f_o = (85 \text{ kHz} \rightarrow 1145 \text{ kHz})$$

4

### Sheet 4

1. A superheterodyne receiver must cover the range from 220 to 224 MHz. The first IF is 10.7 MHz; the second is 1.5 MHz. Find (a) the local oscillator tuning range, (b) the frequency of the second local oscillator, and (c) the first IF image frequency range. (Assume a local oscillator frequency higher than the input by the IF.)

(Sol)  
i)  $220 + 10.7 = 230.7 \text{ MHz}$

$$224 + 10.7 = 234.7 \text{ MHz}$$

Tuning range  $\Rightarrow 230.7$  to  $234.7 \text{ MHz}$

ii)  $2^{\text{nd}} \text{ LO} = 1.5 \text{ MHz higher than the 1st IF}$   
Therefore freq of  $2^{\text{nd}} \text{ LO} = 10.7 + 1.5 = 12.2 \text{ MHz}$

iii)  $230.7 + 10.7 = 241.4 \text{ MHz}$

$$234.7 + 10.7 = 245.4 \text{ MHz}$$

The first IF image frequency range.  $\Rightarrow 241.4 - 245.4 \text{ MHz}$


- =====
2. A dual-conversion superhet has an input frequency of 62 MHz and local oscillators of 71 and 8.6 MHz. What are the two IFs?

(Sol)

The products of the mixers can be the sum or the difference between the local oscillators and the signal. It is more likely though that the first IF is  $71 - 62 = 9 \text{ MHz}$  and the second IF is  $9 - 8.6 = 400 \text{ kHz}$ .

①  $f_c = (220 \rightarrow 224) \text{ MHz}$   $\leftarrow f_{sf1} = 10.7 \text{ MHz}$   
 $f_{sf2} = 1.5 \text{ MHz}$

SOL

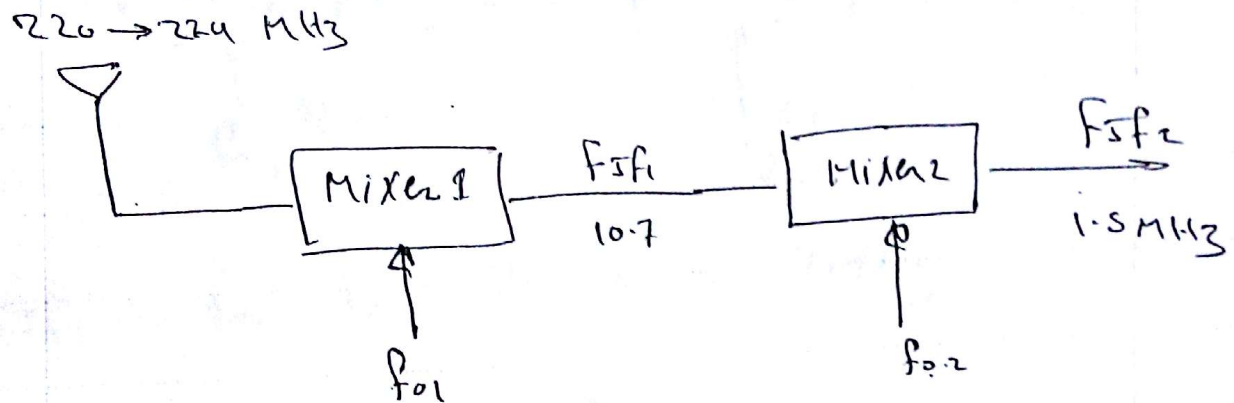

②  $\therefore f_{o1} = f_c + f_{sf1} \Rightarrow f_{o1} = (220 \rightarrow 224) + 10.7$   
 $f_{o1} = 220 + 10.7 \rightarrow 224 + 10.7$   
 $f_{o1} = (230.7 \rightarrow 234.7) \text{ MHz} \Rightarrow \textcircled{a}$

③  $f_{o2} = f_{sf1} + f_{sf2} = 10.7 + 1.5 = 12.2 \text{ MHz} \rightarrow \textcircled{b}$


~~f\_{sf1}~~ ④  $f_{imag} = f_c + 2f_{sf1} = (220 \rightarrow 224) + 2 \times 10.7$   
 $= f_{o1} + 2f_{sf1}$

$f_{img} = (241.4 \rightarrow 245.4) \text{ MHz} \Rightarrow \textcircled{c}$



$$f_c = 62 \text{ MHz} \quad f_{o1} = 71 \text{ MHz} \quad f_{o2} = 8.6 \text{ MHz}$$

SOL

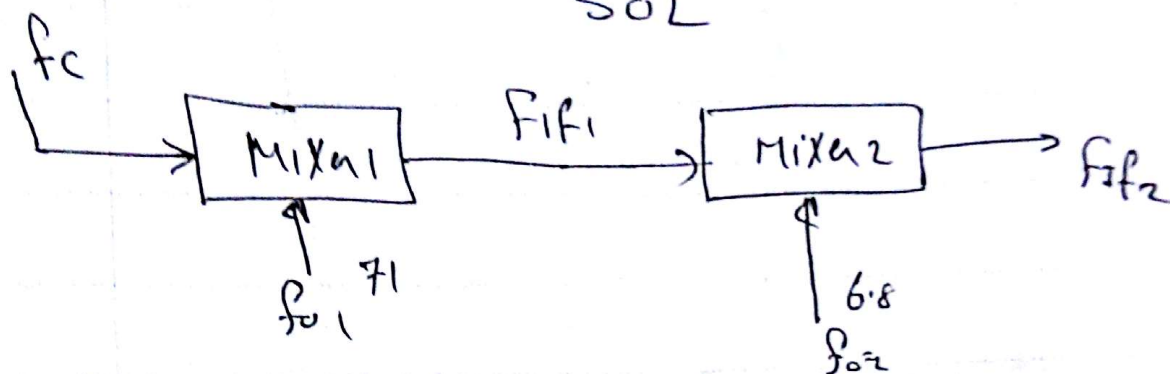

$$f_{if1} = f_{o1} - f_c = 71 - 62 = 9 \text{ MHz}$$

$$f_{if2} = f_{o2} - f_{if1} = f_{if1} - f_{o2} \Rightarrow \text{المهم الزم}$$

بعض النظرة اخرى

$$f_{if2} = |f_{o2} - f_{if1}| = |(8.6 - 9)| = 400 \text{ KHz}$$

ملاحظ

Dual Conversion باستخدام الـ (f\_if1)

قد زادت ضيعة ولبقاء وذا يكون خارج نظام الـ

Bus of the Rf tuned circuit.



Ex Let Bus of tuned circuit is 10 KHz at

Center frequency of 1 MHz  $\therefore f_{if1} = 800 \text{ KHz}$

$\therefore f_{if2} = 455 \text{ KHz}$  - Then  $f_{img} = f_c + 2f_{if1} = 1 + 2 \times 800$

2

= 2.6 MHz

~~ملاحظ~~



بعد دفع نظام ال


Let  $f_c = 100 \text{ MHz}$  &  $f_{sf} = 200 \text{ kHz}$

$$100 \text{ MHz} + 2 \times 200 \text{ MHz} = 100 \text{ MHz}$$

$$= \cancel{100 \text{ MHz}}$$


~~$= 100 \frac{1}{11113}$~~

→ 100.4 MHz

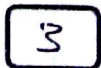
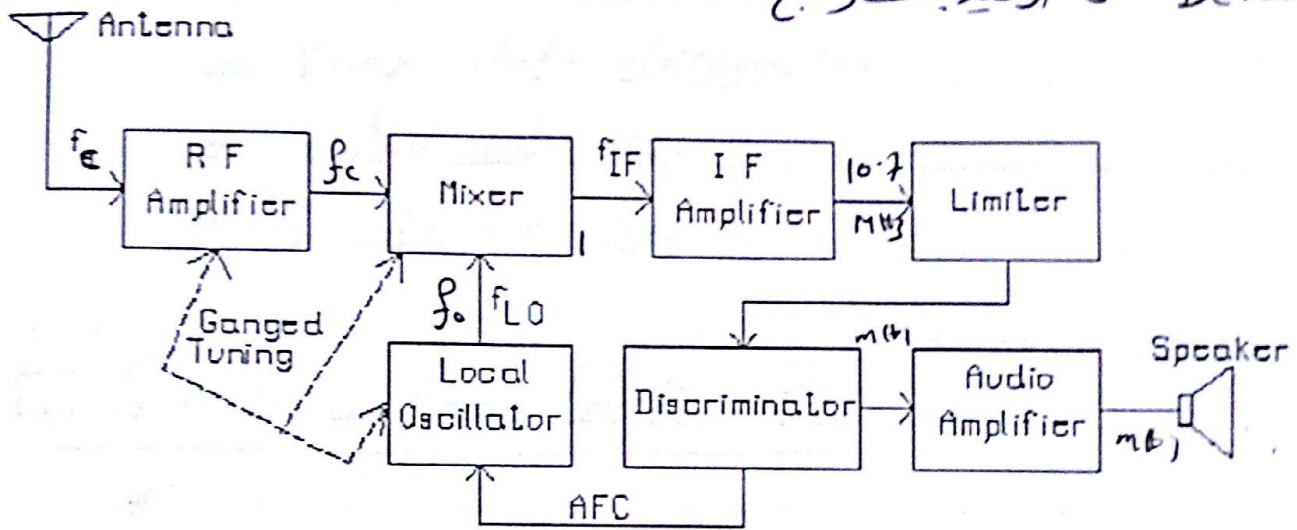
## FM Receiver

ويشبه كثيراً AM Receiver ولكنه يكون الاختلاف في مرحلة الـ Detector أي طريقة استخراج الـ  $m(t)$



limiter : Used to remove noise from Fm signal.

AFC : Automatic Frequency Control

دعويته لظبط تردد الـ  $f_0$  مع الـ Local oscillator وكذلك ضبط الـ RF tuned Circuit عند تردد المحطة المطلوبة لأنه أحياناً يحدث عملية drift لانتشار التغير تأثر التكرار مع المكونات الإلكترونية

## Difference between AM and FM spectrum

|                             | AM                             | FM                           |
|-----------------------------|--------------------------------|------------------------------|
| 1) Range                    | 540 KHz $\rightarrow$ 1600 KHz | 88 MHz $\rightarrow$ 108 MHz |
| 2) $F_{if}$ فقط             | 455 KHz                        | 10.7 MHz                     |
| 3) BW or Carrier separation | 10 KHz                         | 200 KHz                      |



## FM Demodulators :-


- ① phase locked loop (PLL)
- ② slope detection
- ③ phase shift discriminator
- ④ Ratio detection
- ⑤ Quadrature detection

### 1) Phase locked loop PLL

\*

\* is feed back circuit consist of

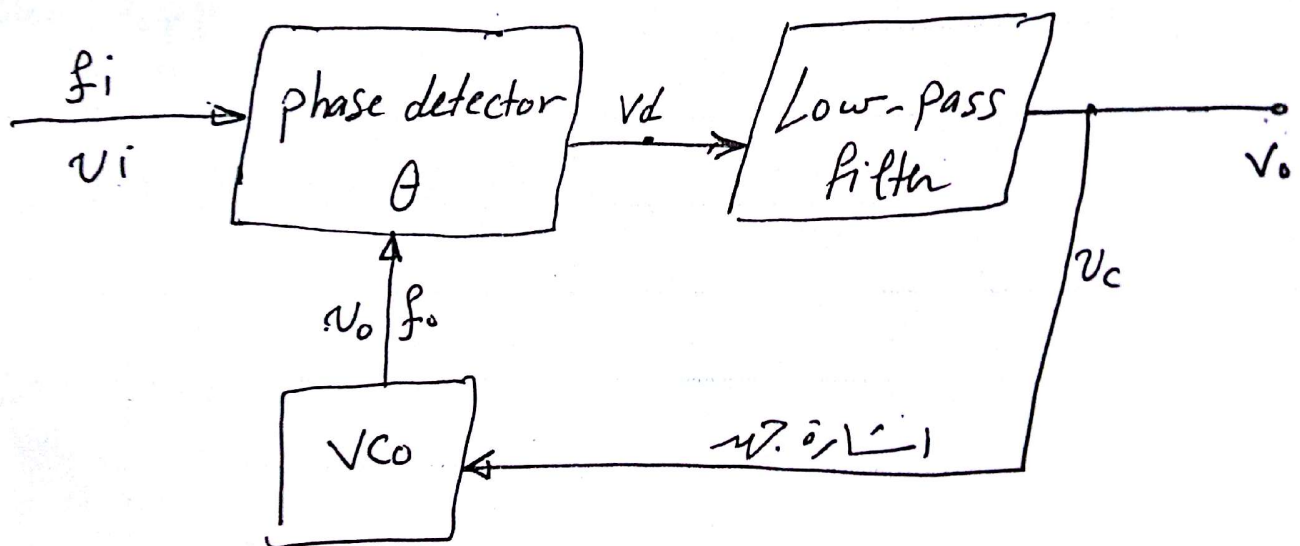- Ⓐ phase detector      Ⓑ Low pass filter      Ⓒ VCO



فكره العمل هي جعل ال  $f_o$  من ال  $v_{co}$  متزامن مع ال  $f_i$  صا تغير حيث  
انه عندما يكون هناك خطأ في ال phase بين ال  $f_i$  و  $f_o$  اي انهم  
متلفين في التردد عندها يزيد او يقل خرج ال phase Detector والذي بدوره  
يغير في تردد ال  $v_{co}$  حتى يتساوى مع تردد ال  $f_i$

## Phase detector :-

هو عبارة عن دائرة تقوم بعملية multiplication  $v_i \times v_o$   $\leftarrow$

\* let

$$v_i = V_i \sin(2\pi f_i t + \theta_i) \rightarrow \text{i/p signal}$$

$$v_o = V_o \sin(2\pi f_o t + \theta_o) \rightarrow \text{From VCO}$$

$$v_d = v_i \times v_o \Rightarrow \text{phase detector o/p}$$

$$v_d = V_i \sin(2\pi f_i t + \theta_i) \times V_o \sin(2\pi f_o t + \theta_o)$$

let  $f_i = f_o \Rightarrow \text{Locking.}$

$$v_d = \frac{V_i V_o}{2} \left[ \underbrace{\cos(\theta_i - \theta_o)}_{\text{الفرق}} - \underbrace{\cos(4\pi f_i t + \theta_i + \theta_o)}_{\text{المجموع}} \right]$$

After Lpf

$$v_c = \frac{V_i V_o}{2} \cos(\theta_i - \theta_o) \quad \therefore (\theta_i - \theta_o) = \theta_e$$

$$\boxed{v_c = \frac{V_i V_o}{2} \cos \theta_e} \quad \text{where } \theta_e = \theta_i - \theta_o$$

$v_c$  :- Control signal from Lpf which feed back to VCO to control its frequency

$\theta_e$  : Phase error

$v_o = \text{VCO o/p}$   $\propto$  proportional to phase difference  $\theta_e$

3

$f_o$  from  $V_{CO}$  depend on  $\theta_e$

$\Rightarrow$  Locking  $\Rightarrow$   $f_i$  قد يطغى نفس تردد  $f_o$  Locking

⑤  $V_{CO}$

هو المكون على إخراج  $f_o$


Variable oscillator

عكس استخدام أي نوع من

أنواع هو المتكامل به Varactor diode

والذي فيه يتم التحكم في  $f_o$  عن طريق جهد عكس يتم تطبيقه على

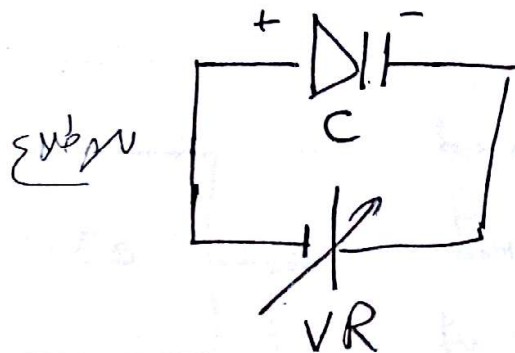ال Varactor diode والذي يتأثر بغيره من الجهد وبالتالي أصبح لدينا مكثف متغير مع الجهد العكس  $V_R$



$$V_R \uparrow \Rightarrow C \downarrow$$

وبالتالي عكس وضع ال Varactor diode في أي دائرة Oscillator  
كثف متغير وبالتالي نستطيع التحكم في تردد المخرج

where

$$f_o = \frac{1}{2\pi RC}$$

$$\text{or } f_o = \frac{1}{2\pi \sqrt{LC}}$$

على حسب شكل الدائرة



when  $V_R$  (Reverse voltage) increase then the capacitance decrease and  $f_o$  increase

$$V_R \uparrow \Rightarrow C \downarrow \Rightarrow f_o \uparrow$$



$$f_o = \frac{1}{2\pi RC}$$

$$f_o = \frac{1}{2\pi \sqrt{LC}}$$

Conversion gain K

$$K = \frac{\Delta f_o}{\Delta V_c} \quad \text{kHz/V}$$

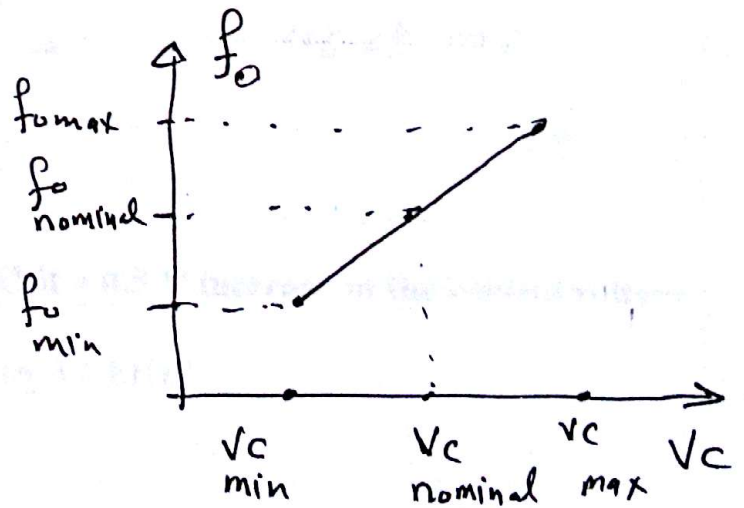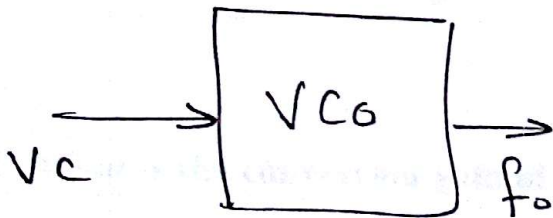عبارة عن مقدار التغير في تردد  $V_c$  نسبة التغير  
حيث  $V_c$  Control volt



Nominal = (nom)  $\Rightarrow$

هي عبارة عن القيمة الاسمية للبيانات أو المعيارية  
أي المتوسط أي خرج ال  $V_c$  بدون زيادة أو نقصان ال  $V_c$

5

## Sheet 5

1. A PLL is locked onto an incoming signal with peak amplitude of 250 mV and a frequency of 10 MHz at a phase angle of  $30^\circ$ . The 400 mV peak VCO signal is at a phase voltage being fed back angle of  $15^\circ$ .

(a) What is the VCO frequency?

(b) What is the value of the control to the VCO at this point?

$$f_i = 10 \text{ MHz} \quad \theta_i = 30^\circ \quad \text{SOL}$$
$$V_i = 250 \text{ mV} \quad \theta_o = 15^\circ \quad V_o = 400 \text{ mV}$$

a) Since PLL is Locked  $\therefore f_i = f_o = 10 \text{ MHz}$

$$b) \therefore V_c = \frac{V_i V_o}{2} \cos \theta_e \quad \theta_e = \theta_i - \theta_o = 30^\circ - 15^\circ = 15^\circ$$

$$\therefore V_c = \frac{250 \times 10^{-3} \times 400 \times 10^{-3}}{2} \cos 15^\circ = 48.29 \text{ mV}$$



2. What is the conversion gain of a VCO if a 0.5 V increase in the control voltage causes the output frequency to increase by 3.6 kHz?

SOL

$$\Delta V_c = 0.5 \text{ V} \quad \Delta f_o = 3.6 \text{ kHz}$$

$$\therefore K = \frac{\Delta f_o}{\Delta V_c} = \frac{3.6 \times 10^3}{0.5} = 7.2 \text{ kHz/V}$$

6

3. If the conversion gain of a certain VCO is 1.5 kHz per volt, how much does the frequency change if the control voltage increases 0.67 V?

SOL

$$K = 1.5 \text{ kHz/V} \quad \Delta f_o = ?? \quad \Delta V_c = 0.67 \text{ V}$$

$$\therefore K = \frac{\Delta f_o}{\Delta V_c} \Rightarrow \Delta f_o = K \cdot \Delta V_c$$

$$\Delta f_o = 1.5 \times 0.67 = 1.005 \text{ kHz}$$






# Basic PLL operation

Case 1-  $f_i = f_o$  &  $\theta_i \neq \theta_o$

Two sinusoidal signals of the same frequency but with a phase difference,

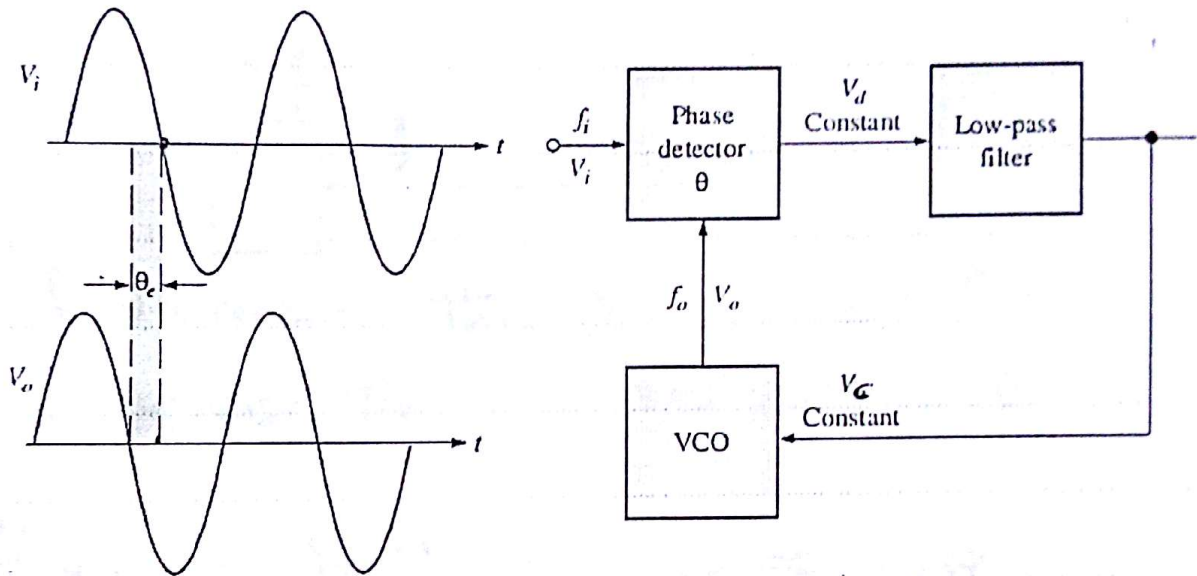For this condition the PLL is in lock and the VCO control voltage is constant.



$\theta_i \neq \theta_o$   $f_i = f_o$   $\theta_e = \theta_i - \theta_o$

$\theta_e = \theta_i - \theta_o = \text{Constant}$

$\therefore V_c = \text{Constant}$

$\therefore \text{PLL is Locking}$

Case 2- If  $f_i$  decreases. (  $f_i < f_o$  )

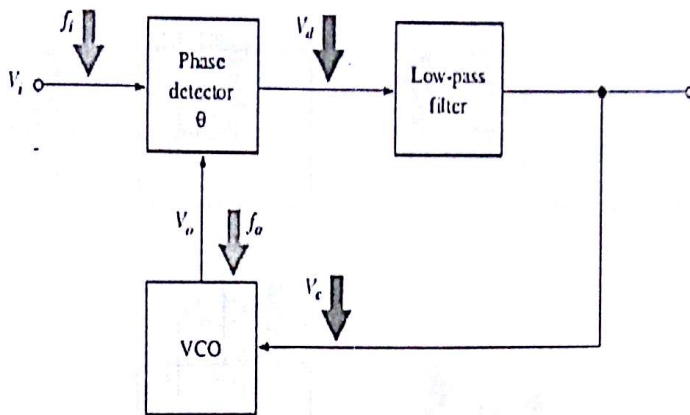



FIGURE 19-44

PLL action when  $f_i$  decreases.

when  $f_i$  decreases then  $\theta_e$  increases to  $\theta_{e1}$   
 then  $V_c$  decrease then  $f_o$  decrease until  $f_o = f_i$

$$\therefore f_i \downarrow \Rightarrow \theta_e \uparrow \Rightarrow V_c \downarrow \Rightarrow f_o \downarrow$$

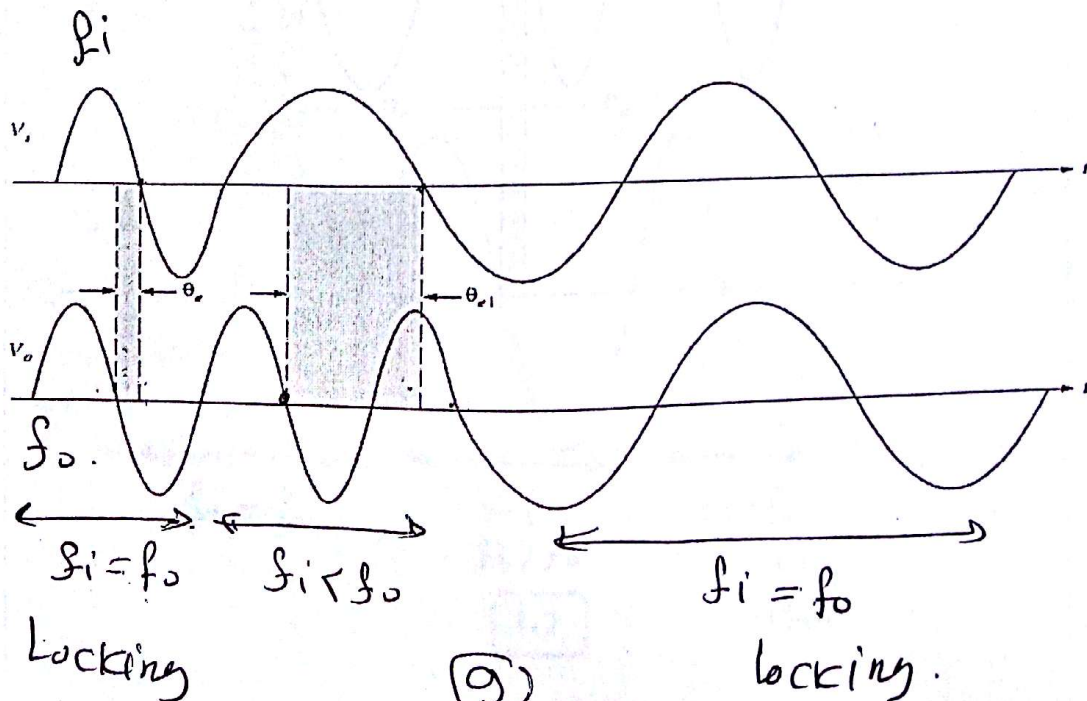مع ان كل الاتي تلاحظ انه عند قلت  $f_i$  بـ كل فاجئ  
 فاجئ  $\theta_e$  زادت دالاتي يقل  $V_c$  والى دوره يقل  
 مع ان  $f_o$  حتى يساوي  $f_i$




(9)

Case 3-


If  $f_i$  increase

$$f_i > f_o$$

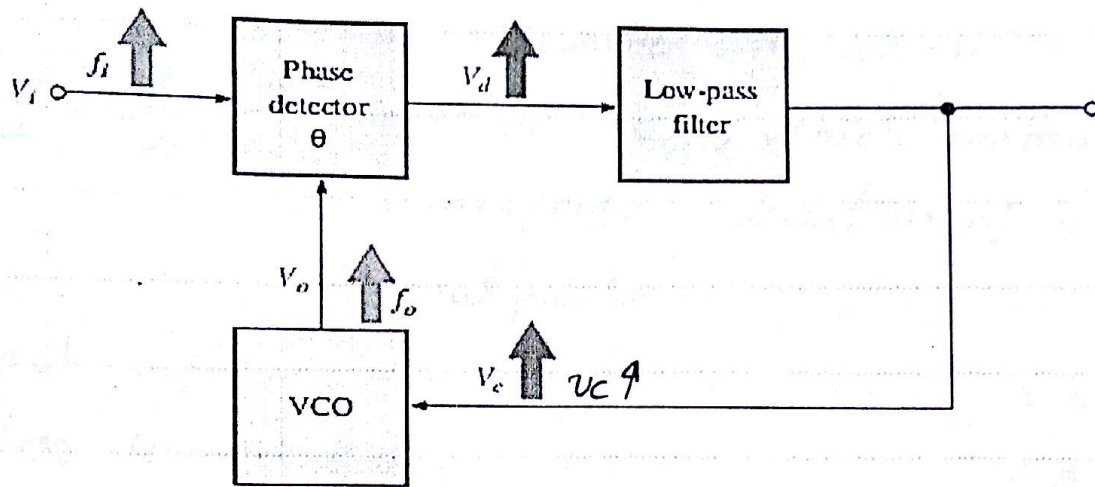when  $f_i$  increase  $\Rightarrow \theta_e$  will decrease to  $\theta_{e1}$  which in turn increase  $V_c$  (VCO Control Voltage) then  $f_o$  increase until  $f_o = f_i$  Locking



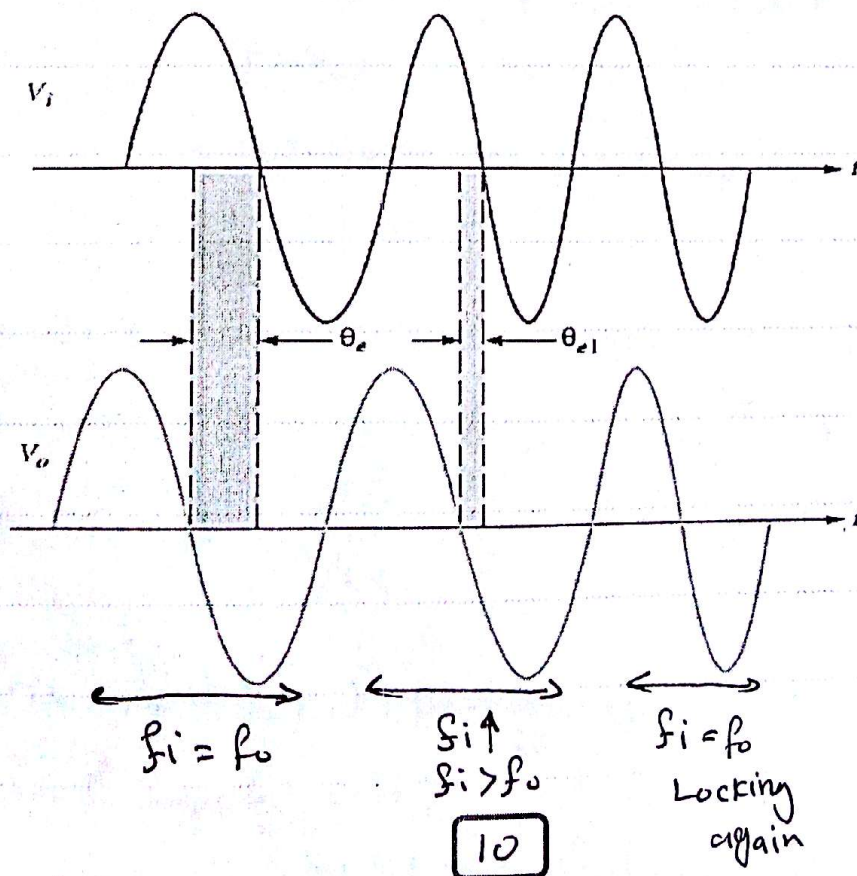$\therefore f_i \uparrow \Rightarrow \theta_e \downarrow \Rightarrow V_c \uparrow \Rightarrow f_o \uparrow \Rightarrow f_o = f_i = \text{Locking}$






تعريف

Lock Range

$$f_{\text{Lock}} = \pm \frac{8f_0}{V_{CC}}$$

⇒ During locking ( $f_i = f_0$ ) is the range of frequencies over which the PLL can maintain lock, which is limited by  
 (i) max frequency deviation of VCO  
 (ii) output limits of phase detector

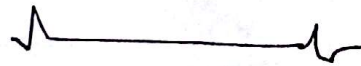في أثناء عملية الـ Locking هو مدى الترددات التي تتبعها PLL فلا  
 (i) max freq deviation of VCO : أقصى انحراف عن عملية Lock  
 (ii) output of phase detector



2) Capture Range

Assuming PLL not Lock is the range of frequencies over which the PLL can acquire «تتبع» Lock with the incoming signal.

هو مدى الترددات التي تتبعها PLL قبل عملية Lock مع الإشارة القادمة  $f_i$

$$f_{\text{Lock}} = \pm \frac{8f_0}{V_{CC}}$$

$f_0$  : Free running frequency of VCO  
 $V_{CC}$  : total supply voltage between +ve and -ve supply